

Memory Structures

Ramon Canal
CTD – Master CANS

Slides based on: Introduction to CMOS VLSI Design. D. Harris



Departament d'Arquitectura
de Computadors

UNIVERSITAT POLITÈCNICA DE CATALUNYA


CTD – Master CANS

Outline

- Memory Arrays
- SRAM Architecture
 - SRAM Cell
 - Decoders
 - Column Circuitry
 - Multiple Ports
- Serial Access Memories




Memory Arrays

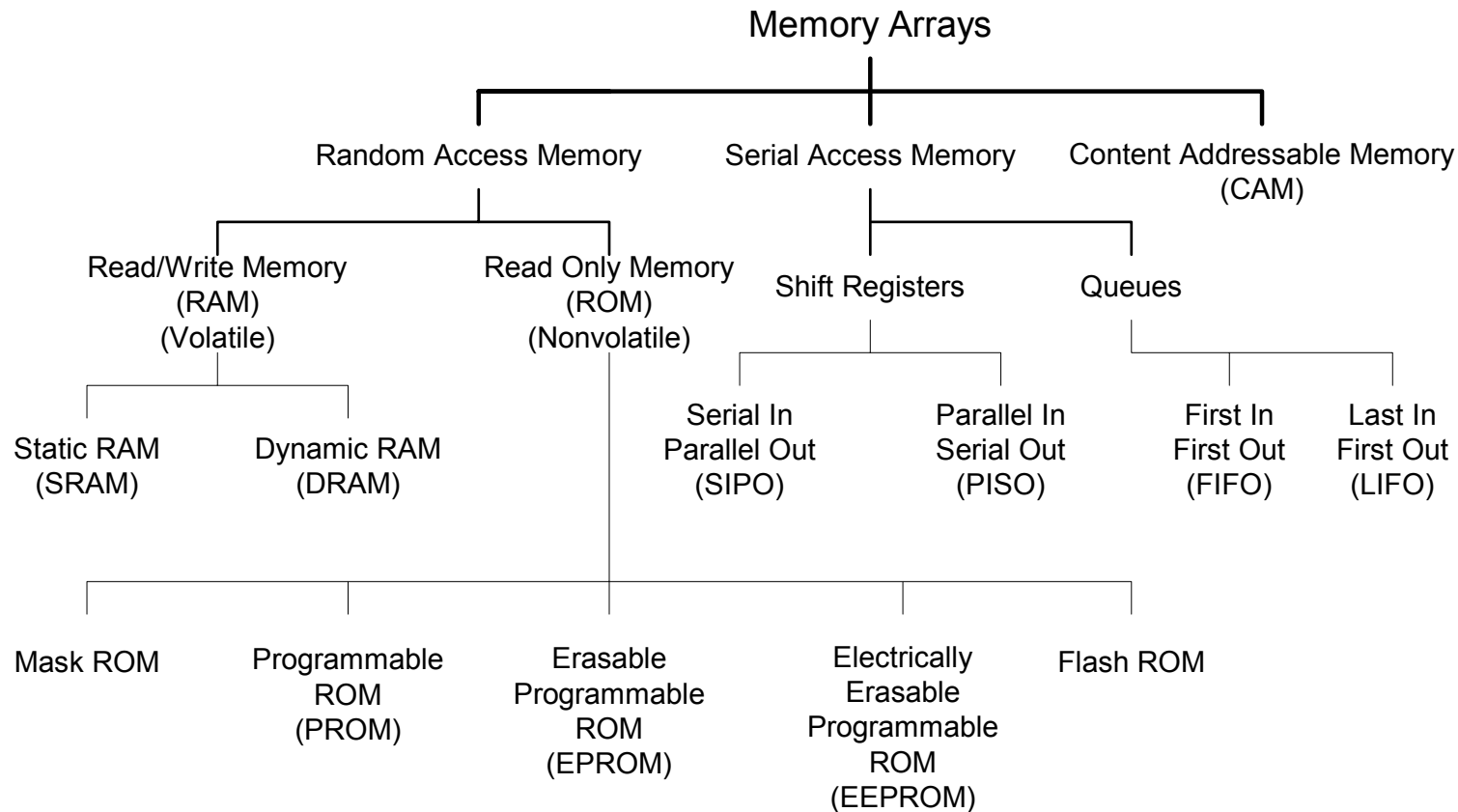

Array Architecture


 
- 2^n words of 2^m bits each
- If $n \gg m$, fold by 2^k into fewer rows of more columns



- Good regularity – easy to design
- Very high density if good cells are used


12T SRAM Cell

  - Basic building block: SRAM Cell
 - Holds one bit of information, like a latch
 - Must be read and written
- 12-transistor (12T) SRAM cell
 - Use a simple latch connected to bitline
 - $46 \times 75 \lambda$ unit cell





6T SRAM Cell

 - Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- Read:
 - Precharge bit, bit_b
 - Raise wordline
- Write:
 - Drive data onto bit, bit_b
 - Raise wordline



SRAM Read

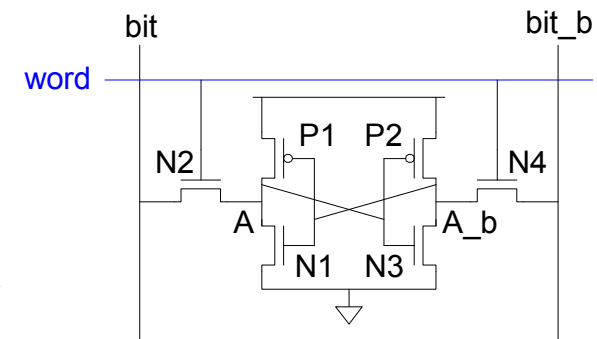
 
- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex: $A = 0$, $A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- *Read stability*
 - A must not flip



CTD – Master CANS

SRAM Read

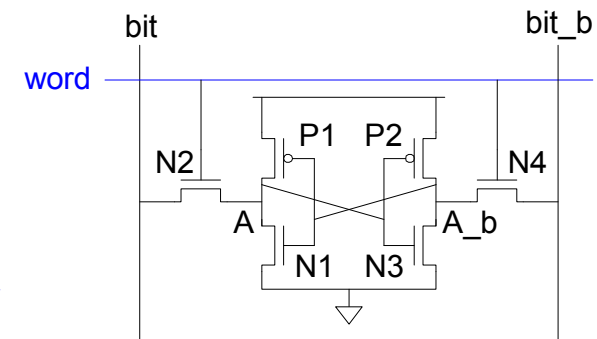
 
- Precharge both bitlines high
- Then turn on wordline
- One of the two bitlines will be pulled down by the cell
- Ex: $A = 0$, $A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- *Read stability*
 - A must not flip
 - $N1 \gg N2$



CTD – Master CANS



SRAM Write

 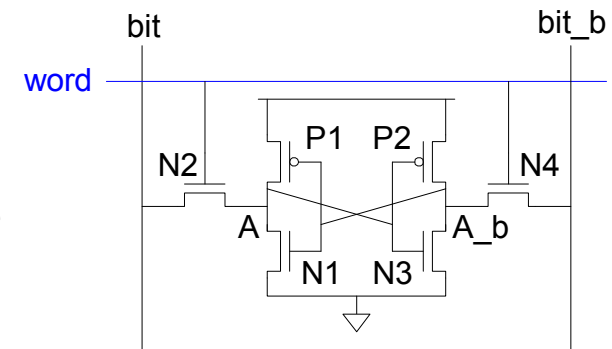- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit_b} = 0$
 - Force A_b low, then A rises high
- *Writability*
 - Must overpower feedback inverter




SRAM Write

 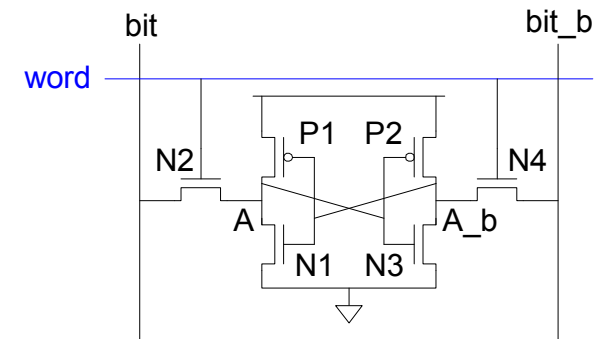- Drive one bitline high, the other low
- Then turn on wordline
- Bitlines overpower cell with new value
- Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit_b} = 0$
 - Force A_b low, then A rises high
- *Writability*
 - Must overpower feedback inverter
 - $N2 \gg P1$




SRAM Sizing

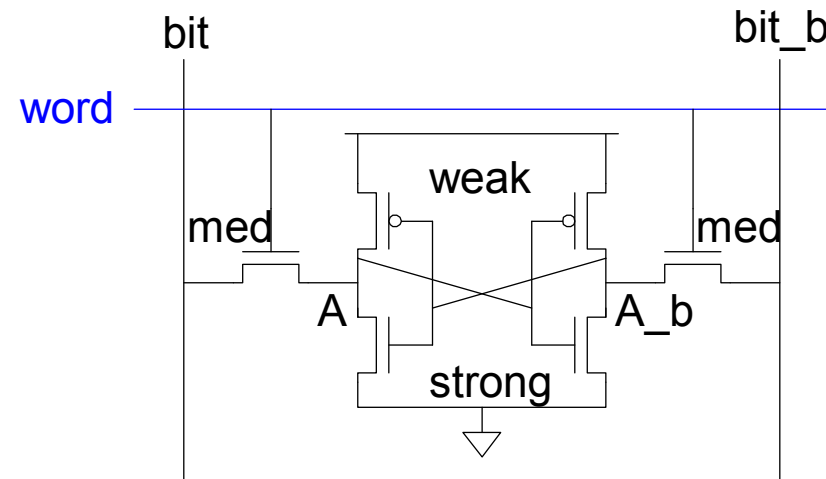- High bitlines must not overpower inverters during reads
- But low bitlines must write new value into cell




SRAM Column Example

Read


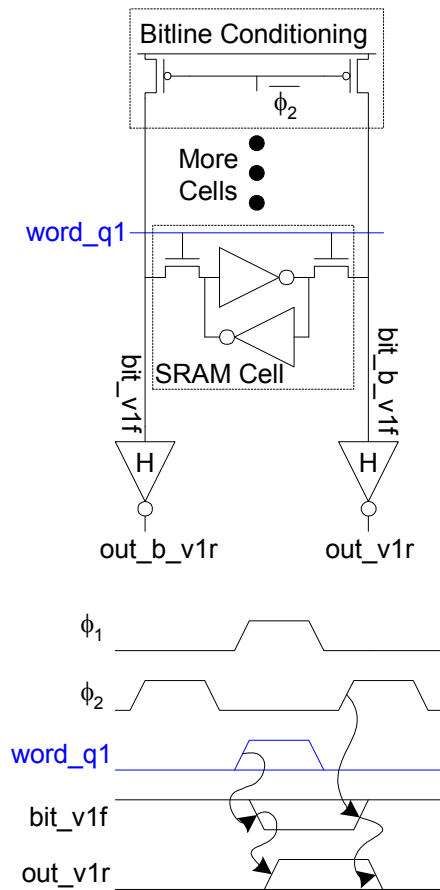


Write

 

SRAM Layout

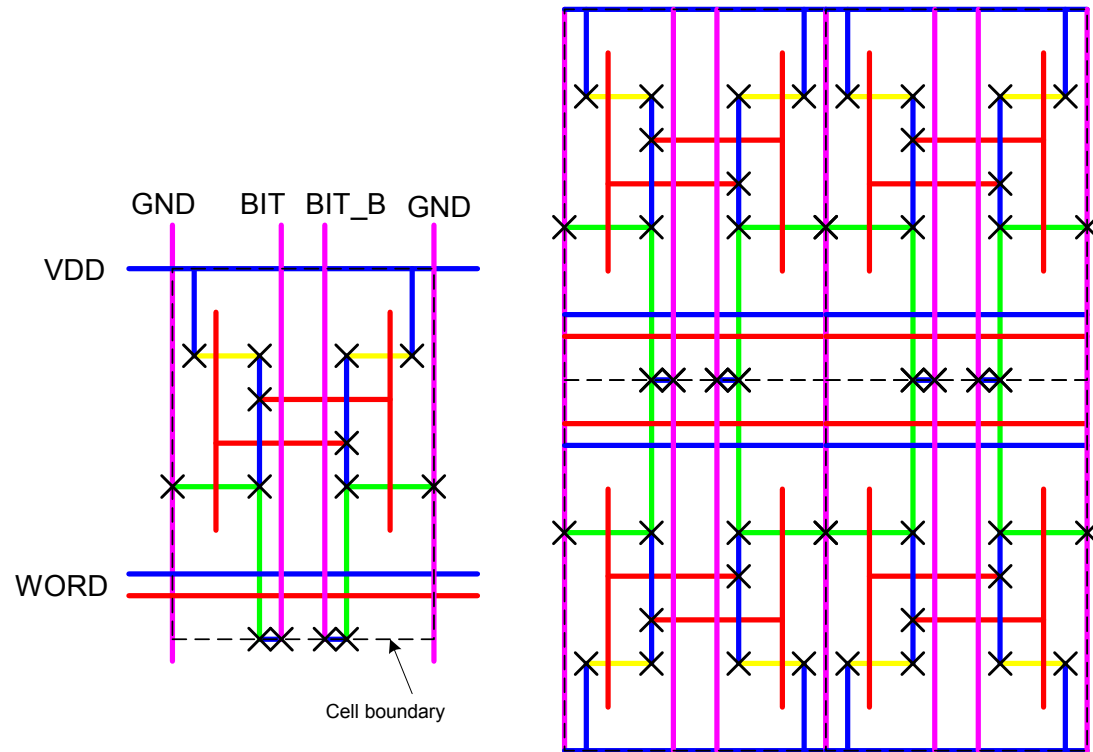 - Cell size is critical: $26 \times 45 \lambda$ (even smaller in industry)
- Tile cells sharing V_{DD} , GND, bitline contacts



Periphery


- ❑ **Decoders**
- ❑ **Sense Amplifiers**
- ❑ **Input/Output Buffers**
- ❑ **Control / Timing Circuitry**




Decoders

- $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates

Static CMOS

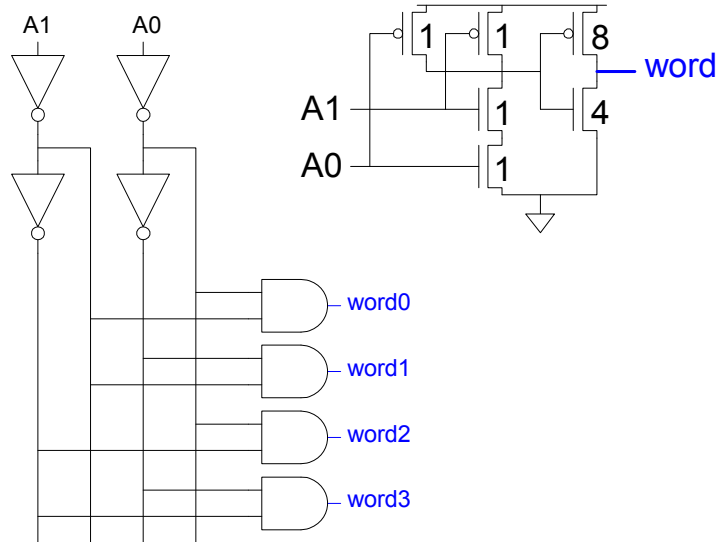


Pseudo-nMOS

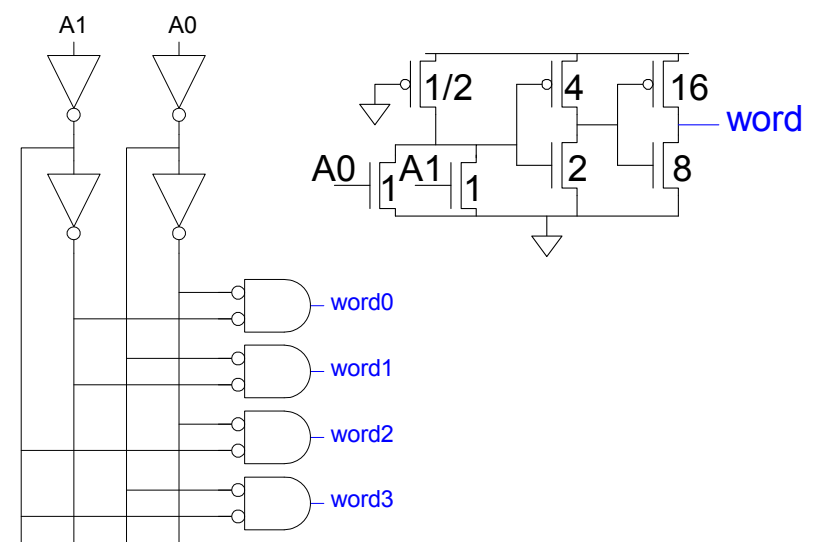


Decoder Layout

 - Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates




Large Decoders

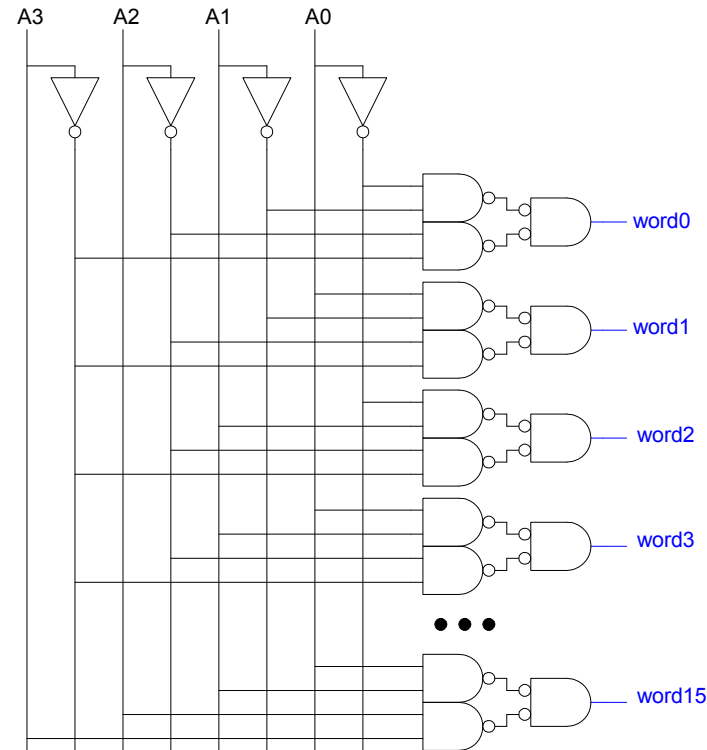- For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

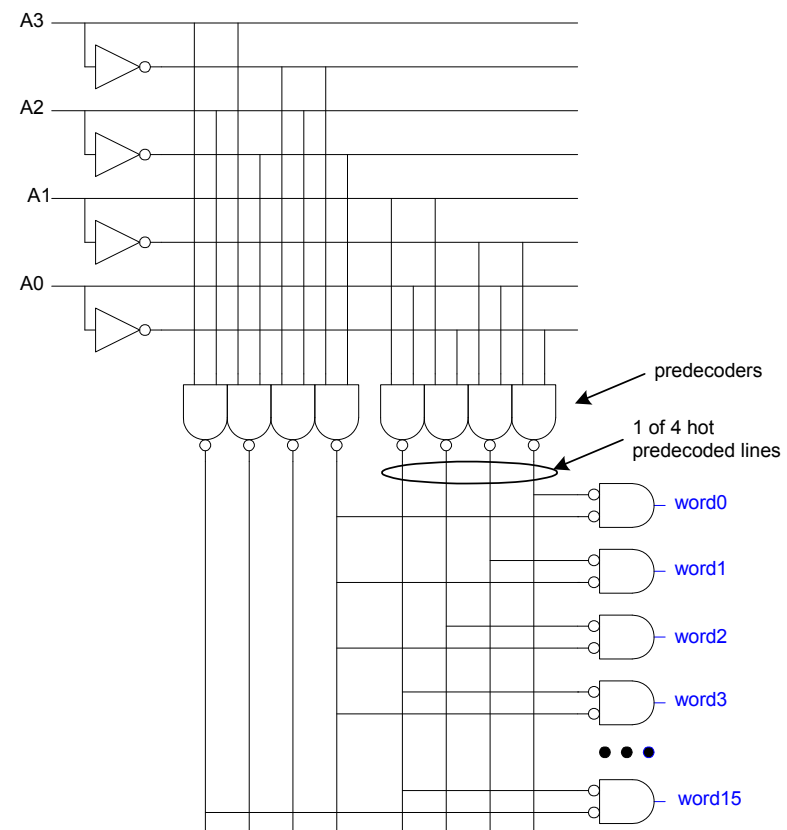- Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area
 - Same path effort



Periphery

- ❑ Decoders
- ❑ **Sense Amplifiers**
- ❑ Input/Output Buffers
- ❑ Control / Timing Circuitry



Sense Amplifiers


$$t_p = \frac{C \cdot \Delta V}{I_{av}}$$

make ΔV as small as possible

large

small

Idea: Use Sense Amplifier

 


Sense Amplifiers

- Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 128 cells on each bitline
- $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- *Sense amplifiers* are triggered on small voltage swing (reduce ΔV)


Differential Pair Amp

 - Differential pair requires no clock
- But always dissipates static power



Clocked Sense Amp

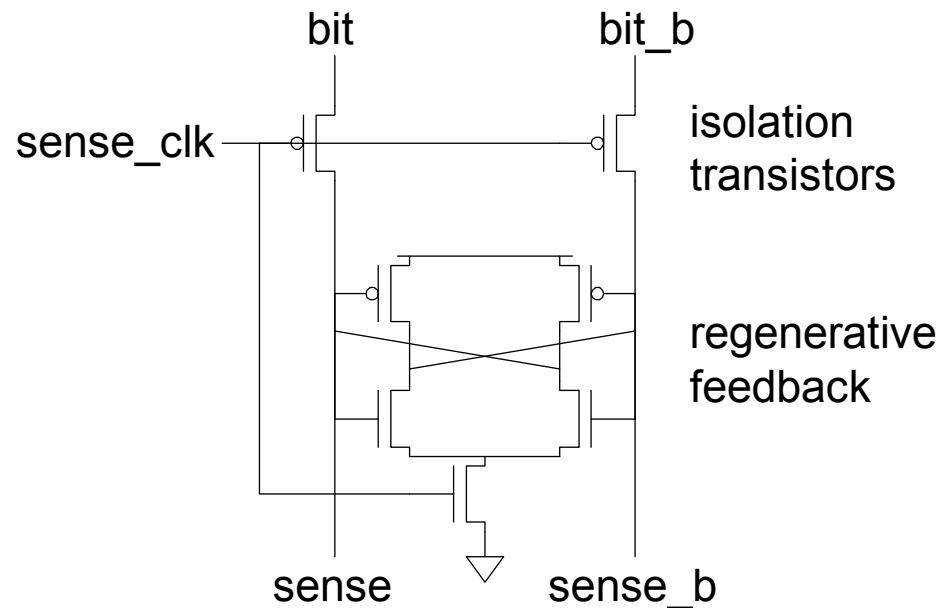- Clocked sense amp saves power
- Requires sense_clk after enough bitline swing
- Isolation transistors cut off large bitline capacitance



Periphery

- ❑ Decoders
- ❑ Sense Amplifiers
- ❑ Input/Output Buffers
- ❑ **Control / Timing Circuitry**




Column Circuitry

- Some circuitry is required for each column
 - Bitline conditioning
 - Column multiplexing




Bitline Conditioning

- Precharge bitlines high before reads

 


 - Equalize bitlines to minimize voltage difference when using sense amplifiers



Twisted Bitlines

 - Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




Column Multiplexing

- Recall that array may be folded for good aspect ratio
- Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers




Tree Decoder Mux

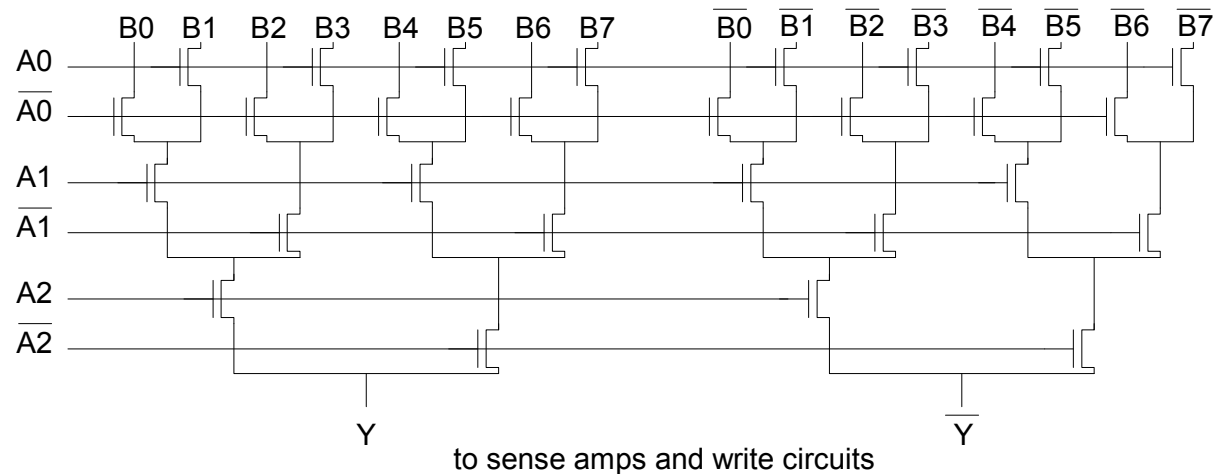- Column mux can use pass transistors
 - Use nMOS only, precharge outputs
- One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed




Single Pass-Gate Mux

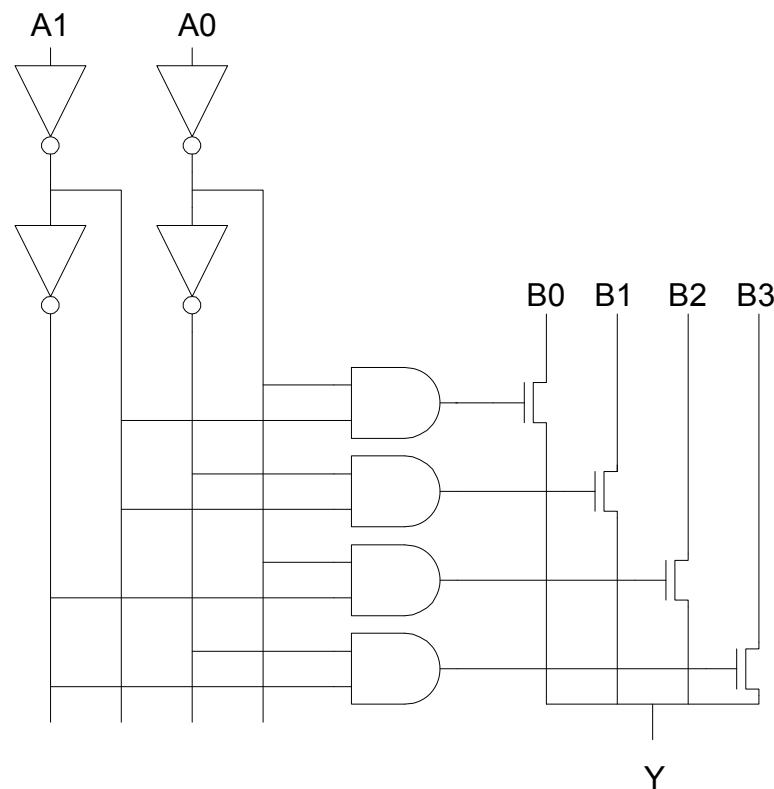- Or eliminate series transistors with separate decoder



Ex: 2-way Muxed SRAM

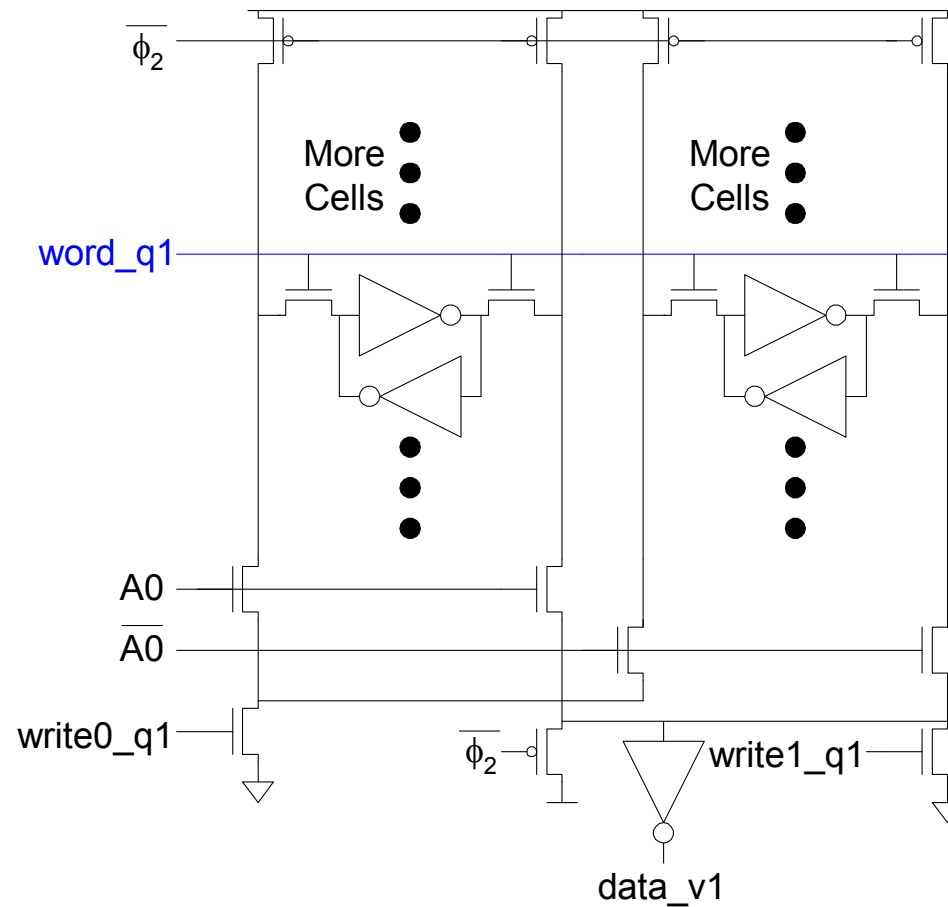

Multiple Ports

- We have considered single-ported SRAM
 - One read or one write on each cycle
- *Multiported* SRAM are needed for register files
- Examples:
 - Multicycle MIPS must read two sources or write a result on some cycles
 - Pipelined MIPS must read two sources and write a third result each cycle
 - Superscalar MIPS must read and write many sources and results each cycle


Memory configuratons

- ❑ **Multiported memories**
- ❑ CAM Memories
- ❑ Serial Access, Queues



Dual-Ported SRAM

 
- Simple dual-ported SRAM
 - Two independent single-ended reads
 - Or one differential write



- Do two reads and one write by time multiplexing
 - Read during ph1, write during ph2

Multi-Ported SRAM

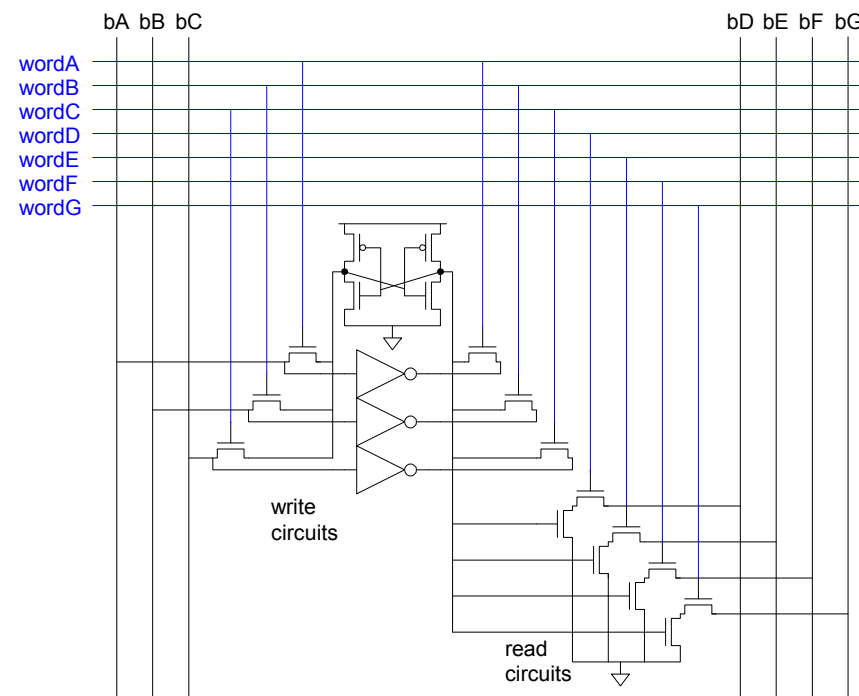- Adding more access transistors hurts read stability
- Multiported SRAM isolates reads from state node
- Single-ended design minimizes number of bitlines




Memory configuratons

- ❑ Multiported memories
- ❑ **CAM Memories**
- ❑ Serial Access, Queues



Contents-Addressable Memory

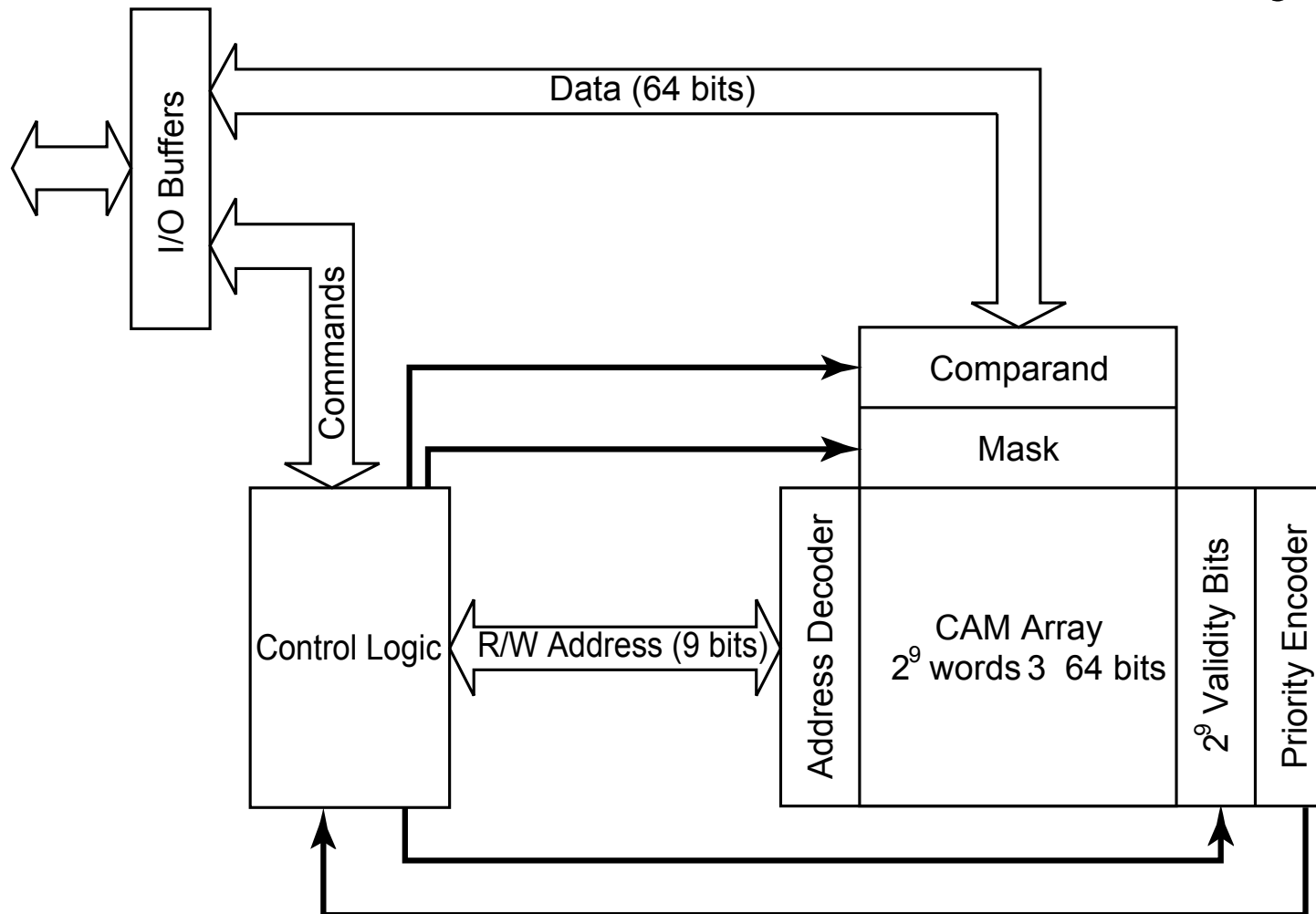

Memory configuratons

- ❑ Multiported memories
- ❑ CAM Memories
- ❑ **Serial Access, Queues**




Serial Access Memories

- Serial access memories do not use an address
 - Shift Registers
 - Tapped Delay Lines
 - Serial In Parallel Out (SIPO)
 - Parallel In Serial Out (PISO)
 - Queues (FIFO, LIFO)




Shift Register

 - *Shift registers* store and delay data
- Simple design: cascade of registers
 - Watch your hold times!




Denser Shift Registers

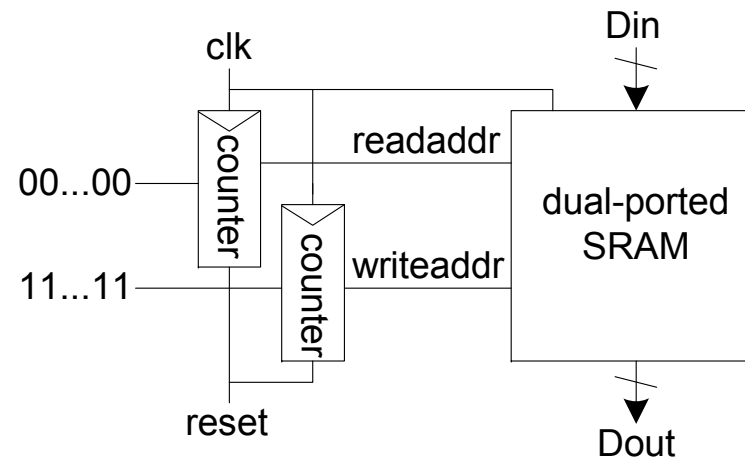- Flip-flops aren't very area-efficient
- For large shift registers, keep data in SRAM instead
- Move read/write pointers to RAM rather than data
 - Initialize read address to first entry, write to last
 - Increment address on each cycle




Tapped Delay Line

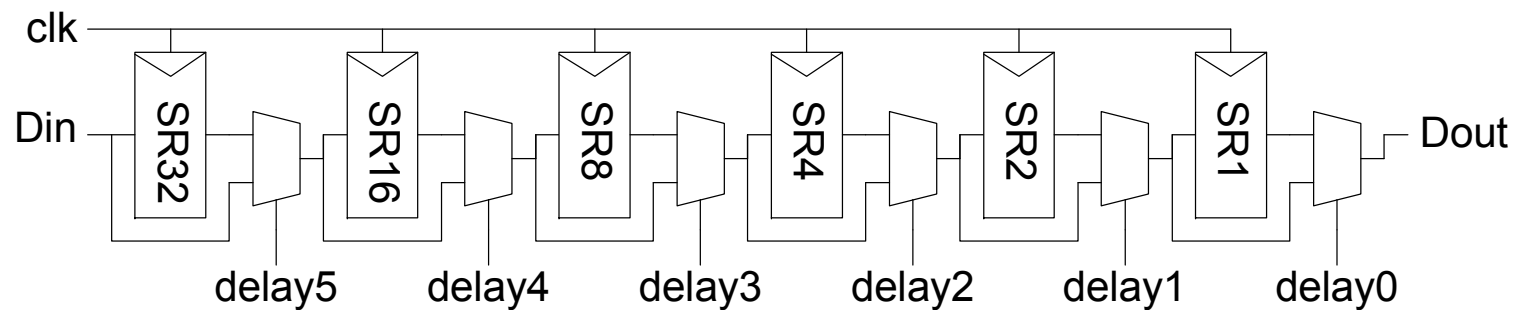- A *tapped delay line* is a shift register with a programmable number of stages
- Set number of stages with delay controls to mux
 - Ex: 0 – 63 stages of delay




Serial In Parallel Out

 - 1-bit shift register reads in serial data
 - After N steps, presents N-bit parallel output




Parallel In Serial Out

 - Load all N bits in parallel when shift = 0
 - Then shift one bit out per cycle



Queues

 - *Queues* allow data to be read and written at different rates.
- Read and write each use their own clock, data
- Queue indicates whether it is full or empty
- Build with SRAM and read/write counters (pointers)



FIFO, LIFO Queues


- *First In First Out (FIFO)*
 - Initialize read and write pointers to first element
 - Queue is EMPTY
 - On write, increment write pointer
 - If write almost catches read, Queue is FULL
 - On read, increment read pointer
- *Last In First Out (LIFO)*
 - Also called a *stack*
 - Use a single *stack pointer* for read and write

Other considerations


- ☐ **Leakage control**
- ☐ **Redundancy**
- ☐ **Flash Memories**



Suppressing Leakage in SRAM

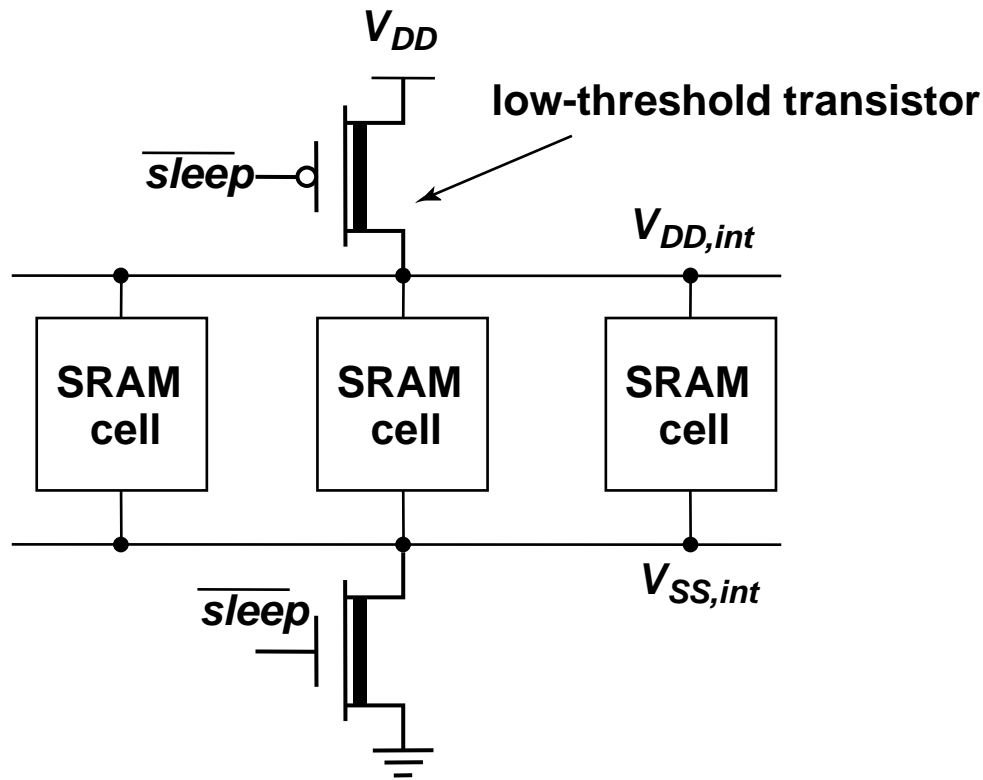

Inserting Extra Resistance

 


Reducing the supply voltage

Other considerations

- ☐ Leakage control
- ☐ **Redundancy**
- ☐ Flash Memories



Redundancy

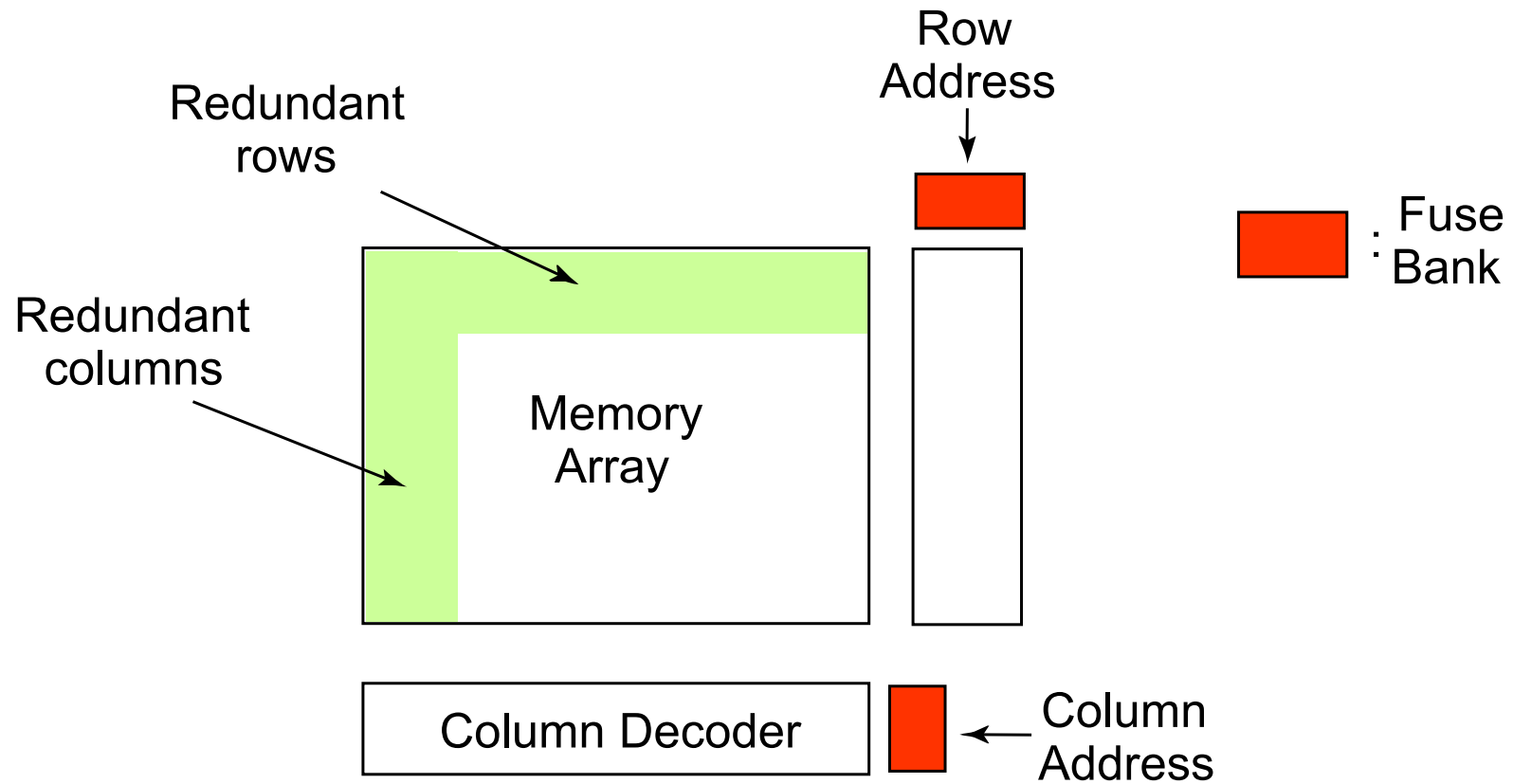

Error-Correcting Codes

Example: Hamming Codes

$P_1 P_2 B_3 P_4 B_5 B_6 B_7$

e.g. B3 Wrong

with

$$P_1 \oplus B_3 \oplus B_5 \oplus B_7 = 0$$

1

$$P_2 \oplus B_3 \oplus B_6 \oplus B_7 = 0$$


1

= 3

$$P_4 \oplus B_5 \oplus B_6 \oplus B_7 = 0$$

0

Redundancy and Error Correction

 


Other considerations

- ☐ Leakage control
- ☐ Redundancy
- ☐ **Flash Memories**




Flash EEPROM

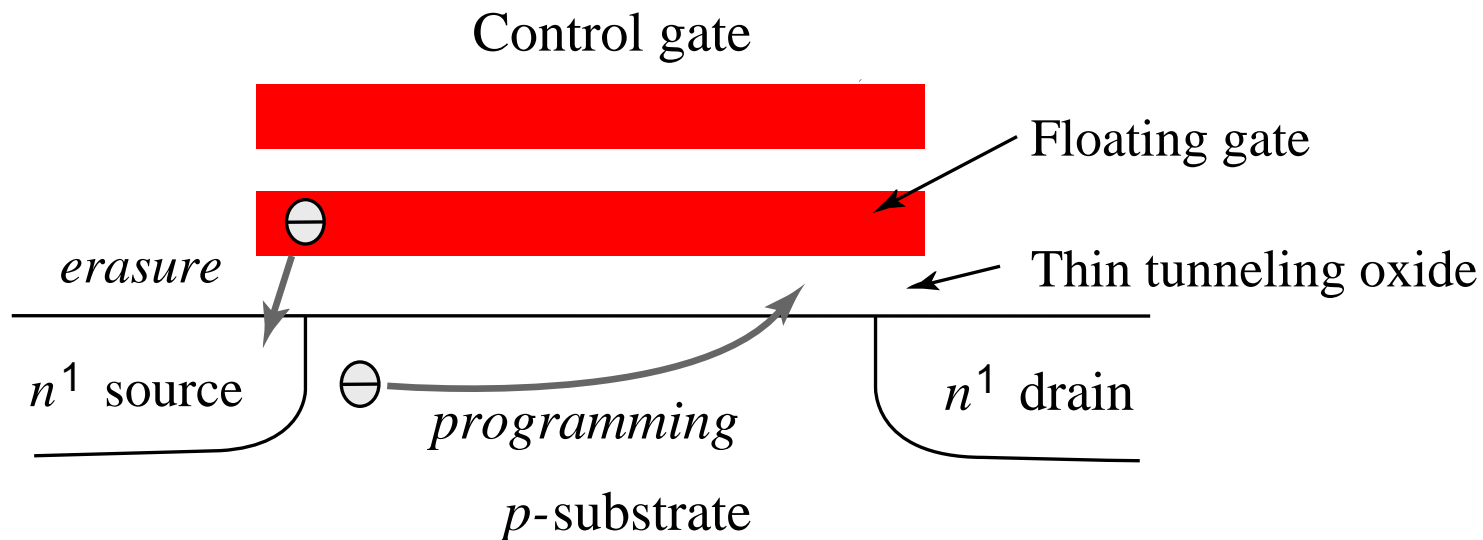

Many other options ...

Cross-sections of NVM cells

 

Flash

EPROM





Departament d'Arquitectura
de Computadors



UNIVERSITAT POLITÈCNICA DE CATALUNYA

CTD – Master CANS
Courtesy Intel

  
Basic Operations in a NOR Flash Memory— Erase



  
Basic Operations in a NOR Flash Memory— Write



Basic Operations in a NOR Flash Memory—

 


Read

 

Conclusions

Memory Structure:

 

CTD – Master CANS